



Year 4
Topic: Electricity
Strand: Physics

What I should already know.

- **Electricity** is a form of **energy** that can be carried by wires and is used for heating and lighting, and to provide **power** for **devices**.
- **Sources** of light and sound may need **electricity** to work.

What will I know by the end of the unit?

Where does **electricity** come from?

- **Electricity** is **generated** using **energy** from natural **sources** such as the **Sun**, **oil**, **water** and **wind**.
- These can also be called **fuel sources**.

What are **electrical conductors** and **insulators**?

- When objects are placed in the **circuits**, they may or may not allow **electricity** to pass through.
- Objects that are made from materials that allow **electricity** to pass through a create a complete **circuit** are called **electrical conductors**.
- Objects that are made from materials that do not allow **electricity** to pass through and do not complete a **circuit** are called **electrical insulators**.


How does a **circuit** work?

- A **complete circuit** is a **loop** that allows **electrical current** to flow through **wires**.
- A **circuit** contains a **battery**, **(cell)**, **wires** and an **appliance** that requires **electricity** to work (such as a **bulb**, **motor** or **buzzer**).
- The **electrical current** flows through the wires from the **battery (cell)** to the **bulb**, **motor** or **buzzer**.
- A **switch** can break or reconnect a **circuit**.
- A **switch** controls the flow of the **electrical current** around the **circuit**. When the **switch** is off, the **current** cannot flow. This is not the same as an incomplete **circuit**.


Vocabulary

Appliances	A device or machine in your home that you use to do a job such as cleaning or cooking. Appliances are often electrical.
Battery	Small devices that provide the power for electrical items such as torches.
Bulb	The glass part of an electric lamp, which gives out light when electricity passes through it.
Buzzer	An electrical device that is used to make a buzzing sound.
Cell	A synonym for battery .
Circuit	A complete route which an electric current can flow around.
Component	The parts that something is made of.
Conductor	A substance that heat or electricity can pass through or along.
Current	A flow of electricity through a wire or circuit .
Device	An object that has been invented for a particular purpose.
Electricity	A form of energy that can be carried by wires and in used for heating and lighting, and to provide power for devices .
Energy	The power from sources such as electricity that makes machines work or provides heat.
Fuel	A substance such as coal, oil, or petrol that is burned to provide heat or power .
Generate	Cause it to begin and develop.
Insulator	A non- conductor of electricity or heat.
Mains	Where the supply of water, electricity , or gas enters a building.
Motor	A device that uses electricity or fuel to produce Movement.
Power	Power is energy , especially electricity , that is obtained in large quantities from a fuel source and used to operate lights, heating, and machinery.
Source	Where something comes from.
Switch	A small control for an electrical device which you use to turn the device on or off.
Wires	A long thin piece of metal that is used to fasten things or to carry electric current .

Diagram - Circuits

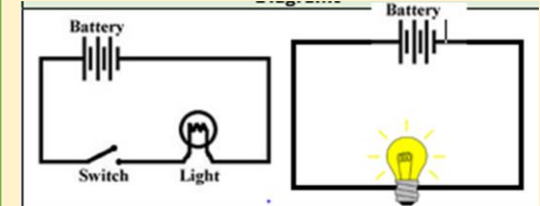

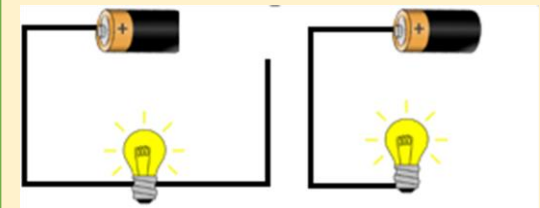These are complete **circuits** - they have a **battery (cell)** and a **component (bulb)**. The **wires** are placed in the right places of the **battery** for the **circuit** to work.



These **circuits** will not work as they are incomplete.

Diagrams – Electrical appliances

Which **appliances** run on **electricity**?

- Some **appliances** use **batteries** and some use **mains electricity**.
- **Batteries** come in different sizes depending on how much and for how long the **appliance** is used.
- Common **appliances** that use **electricity**.

